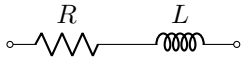


Lecture 31, Mar 30, 2022

Impedance of RL, RC, LC, and RLC circuits


- For an RL circuit:



$$- \mathbf{Z}_{RL} = \mathbf{Z}_R + \mathbf{Z}_L = R + j\omega L$$

- * The real part of the impedance for an RL circuit is the resistance of the resistor; the imaginary part is ωL , frequency times the inductance of the inductor
- * Combining R and L gives both a resistance and a reactance
- * The angle depends on both R and L ; if $\mathbf{Z}_R \gg \mathbf{Z}_L$ then $\angle \mathbf{Z}_{RL} \rightarrow 0$; if $\mathbf{Z}_R \ll \mathbf{Z}_L$ then $\angle \mathbf{Z}_{RL} \rightarrow 90^\circ$
- * The phase difference is $0 < \theta_v - \theta_i < 90^\circ$; greater resistance leads to less phase difference, while greater inductance leads to more phase difference
- * Voltage leads current by some amount between 0° and 90°


- For an RC circuit:

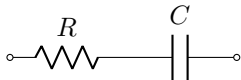

$$- \mathbf{Z}_{RC} = \mathbf{Z}_R + \mathbf{Z}_C = R - \frac{j}{\omega C}$$

- * This time the angle is between 0° and 90° since the imaginary part (reactance) is negative
- * $\mathbf{Z}_R \gg \mathbf{Z}_C \implies \angle \mathbf{Z}_{RC} \rightarrow 0$ and $\mathbf{Z}_R \ll \mathbf{Z}_C \implies \angle \mathbf{Z}_{RC} \rightarrow -90^\circ$
- * Voltage lags current by some amount between 0° and 90° (current leads voltage)


- For an LC circuit:

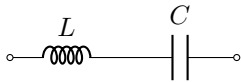

$$- \mathbf{Z}_{LC} = \mathbf{Z}_L + \mathbf{Z}_C = j \left(\omega L - \frac{1}{\omega C} \right)$$

- * The impedance of an LC circuit is entirely imaginary (no resistance)
- * The imaginary part can be positive or negative, depending on the relative values of the inductance and capacitance
 - $\omega L > \frac{1}{\omega C} \implies \text{Im } \mathbf{Z}_{LC} > 0$, and voltage leads current by 90°
 - $\omega L < \frac{1}{\omega C} \implies \text{Im } \mathbf{Z}_{LC} < 0$, and voltage lags current by 90°

- For an RLC circuit:

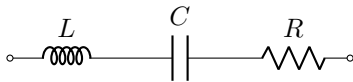


$$- \mathbf{Z}_{RLC} = \mathbf{Z}_R + \mathbf{Z}_C + \mathbf{Z}_L = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

- * The real part is positive, the imaginary part can be positive or negative depending on the relative values of inductance and capacitance
- * The angle is between -90° and 90° ; sign follows the same pattern as for an LC circuit

Sinusoidal Steady State Analysis

- Since all the laws and techniques (KVL, KCL, etc) still hold in the phasor domain, we can analyze AC circuits in the same way
- Convert the circuit into phasor domain (resistances, inductances, and capacitances to impedances), and use $\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}}$ in the same way that $R = \frac{v}{i}$ is used in DC circuits
 - Convert the phasors back to time domain afterwards if desired
- The only difference is that complex phasors are used instead of real numbers

- Example:

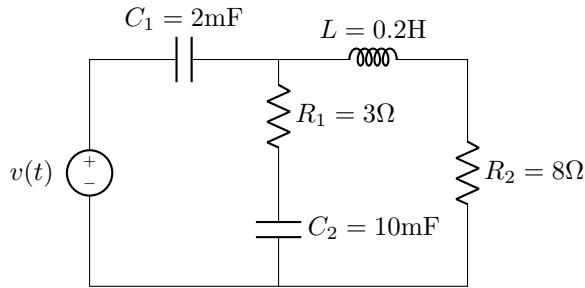

- $v(t) = 20 \cos(50t)V$, find $i(t)$


* Convert the voltage to a phasor: $\mathbf{V} = 20\angle 0^\circ$

* For the 2mF capacitor, $\mathbf{Z}_1 = \frac{-j}{\omega C_1} = \frac{-j}{50 \cdot 2 \times 10^{-3}} = -j10\Omega$

* For the series RC connection in the middle, $\mathbf{Z}_2 = R_1 - \frac{j}{\omega C_2} = 3 - \frac{j}{50 \cdot 10 \times 10^{-3}} = 3 - j2\Omega$

* For the series RL connection, $\mathbf{Z}_3 = R_2 + j\omega L = 8 + j50 \cdot 0.2 = 8 + j10\Omega$

* In the phasor domain:

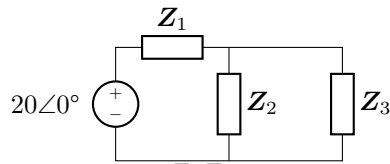

* $\mathbf{Z}_{eq} = \mathbf{Z}_1 + \frac{\mathbf{Z}_2 \mathbf{Z}_3}{\mathbf{Z}_2 + \mathbf{Z}_3} = 3.22 - j11.07\Omega = 11.53\angle -73.5^\circ$

* $\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{20\angle 0^\circ}{11.53\angle -73.5^\circ} = 1.73\angle 73.5^\circ \text{A}$

* Back to the time domain, $i(t) = 1.73 \cos(50t + 73.5^\circ)$